

PHYS 205-Section 03
Electricity and Magnetism - Winter 2018
Assignment 6 – Solution

1. A solenoid having an inductance of 6.30 mH is connected in series with a $1.20\text{ k}\Omega$ resistor. (a) If a 14 V battery is connected across the pair, how long will it take for the current through the resistor to reach 80% of its final value? **(3 points)**
(b) What is the current through the resistor at time $t = 1\tau_L$? **(2 points)**

Solution:

(a) If the battery is switched into the circuit at $t = 0$, then the current at a later time t is given by

$$i = \frac{\mathcal{E}}{R}(1 - e^{-t/\tau_L}) ,$$

where $\tau_L = L/R$. Our goal is to find the time at which $i = 0.800\mathcal{E}/R$. This means

$$0.800 = 1 - e^{-t/\tau_L} \Rightarrow e^{-t/\tau_L} = 0.200 .$$

Taking the natural logarithm of both sides, we obtain $-(t/\tau_L) = \ln(0.200) = -1.609$. Thus,

$$t = 1.609\tau_L = \frac{1.609L}{R} = \frac{1.609(6.30 \times 10^{-6}\text{ H})}{1.20 \times 10^3\ \Omega} = 8.45 \times 10^{-9}\text{ s} .$$

(b) At $t = 1.0\tau_L$ the current in the circuit is

$$i = \frac{\mathcal{E}}{R}(1 - e^{-1.0}) = \left(\frac{14.0\text{ V}}{1.20 \times 10^3\ \Omega} \right) (1 - e^{-1.0}) = 7.37 \times 10^{-3}\text{ A} .$$

2. An alternating source drives a series RLC circuit with an emf amplitude of 6 V , at a phase angle of $+30.0^\circ$. When the potential difference across the capacitor reaches its maximum positive value of $+5\text{ V}$, what is the potential difference across the inductor (sign included)? **(5 points)**

Solution:

Drawing the phase diagram, like the one in your textbook leads to:

$$V_L - V_C = (6.00\text{ V})\sin(30^\circ) = 3.00\text{ V} .$$

With the magnitude of the capacitor voltage at 5.00 V , this gives a inductor voltage magnitude equal to 8.00 V . Since the capacitor and inductor voltage phasors are 180° out of phase, the potential difference across the inductor is -8.00 V .

3. An air conditioner connected to a 120 V rms AC line is equivalent to a $12\ \Omega$ resistance and a $1.30\ \Omega$ inductive reactance in series. Calculate
- the impedance of the air conditioner (**3 points**)
 - the average rate at which energy is supplied to the appliance (**2 points**)

Solution:

(a)

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(12.0\ \Omega)^2 + (1.30\ \Omega - 0)^2} = 12.1\ \Omega.$$

(b) The average rate at which energy has been supplied is

$$P_{\text{avg}} = \frac{\varepsilon_{\text{rms}}^2 R}{Z^2} = \frac{(120\text{ V})^2 (12.0\ \Omega)}{(12.07\ \Omega)^2} = 1.186 \times 10^3\text{ W} \approx 1.19 \times 10^3\text{ W}.$$

4. A plane electromagnetic wave of intensity $6\frac{\text{W}}{\text{m}^2}$, moving in the x direction, strikes a small perfectly reflecting pocket mirror, of area 40 cm^2 , held in the yz plane.
- What momentum does the wave transfer to the mirror each second? (**0 points**)
 - Find the force the wave exerts on the mirror. (**0 points**)

Solution:

(a) The magnitude of the momentum transferred to the assumed totally reflecting surface in time interval Δt is (from Equation 34.29)

$$\Delta p = \frac{2T_{\text{ER}}}{c} = \frac{2SA\Delta t}{c}$$

Then the momentum transfer is

$$\Delta \vec{p} = \frac{2\vec{S}A\Delta t}{c} = \frac{2(6.00\ \hat{i}\text{ W/m}^2)(40.0 \times 10^{-4}\text{ m}^2)(1.00\text{ s})}{3.00 \times 10^8\text{ m/s}}$$

$$\Delta \vec{p} = \boxed{1.60 \times 10^{-10}\ \hat{i}\text{ kg} \cdot \text{m/s each second}}$$

(b) The force is

$$\vec{F} = PA\hat{i} = \frac{2SA}{c}\hat{i} = \frac{2(6.00\text{ W/m}^2)(40.0 \times 10^{-4}\text{ m}^2)(1.00\text{ s})}{3.00 \times 10^8\text{ m/s}}$$

$$= \boxed{1.60 \times 10^{-10}\ \hat{i}\text{ N}}$$

(c) The answers are the same. Force is the time rate of momentum transfer.